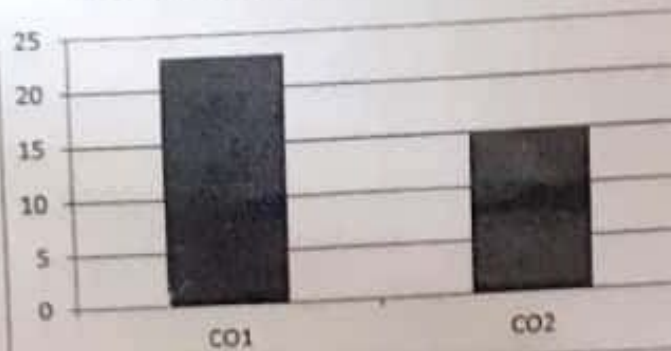


7	<p>Calculate the current delivered by battery in the given circuit using Star-Delta Transform</p>	[5]	1	L3
8	<p>Calculate the average and r.m.s value of following voltage wave form</p>	[5]	2	L3
9	<p>Solve for V in the given circuit with the help of Superposition theorem</p>	[5]	1	L3


CO wise marks distribution



Bloom's distribution



- L1 Remember
- L2 Understand
- L3 Apply
- L4 Analyze

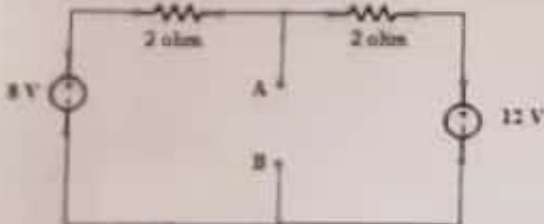UNITED COLLEGE OF ENGINEERING & RESEARCH				Department of Electrical Engineering		
1 st SESSIONAL EXAM		SEMESTER: 1 st		SECTION : H I J K L M		Jan- 2021
TIME: 2hrs		SUBJECT: BASIC ELECTRICAL ENGG.		Paper code: KEE 101		MM. 30
READ ALL INSTRUCTIONS AND QUESTIONS VERY CAREFULLY						
SECTION A (Attempt ALL questions) Short answer						
1	a	Is 'L' a linear element? Explain the answer	[6]	CO	Bloom's Level	
1	b	Define Ideal Voltage and Current source	[1]	1	L2	
1	c	Define Bilateral & Unilateral Elements with example	[1]	1	L1	
1	d	Identify what is the reciprocal of inductive reactance and its unit?	[1]	1	L1	
1	e	Enlist the limitations of Ohm's law.	[1]	2	L1	
1	f	State Thevenin's and Norton's Theorem.	[1]	1	L1	
SECTION B (Attempt ANY THREE questions) Medium answer						
2	Demonstrate that in a purely resistive circuit consumed power is always positive.		[9]			
3	Compare the circuit with the Norton's equivalent at terminal AB. Determine the current through 4 ohm resistor across AB.		[3]	1	L4	
						
4	Explain Active, Reactive and Apparent powers with proper explanation and units. Also discuss power factor in AC circuits.		[3]	2	L2	
5	A 100V, 80W lamp is to be operated on 230V, 50Hz AC supply. Calculate the inductance to be connected in series with the lamp for the above operation. Lamp can be taken as pure resistance.		[3]	2	L3	
SECTION C (Attempt ANY THREE question) Long answer						
6	Compare the given circuit with the equivalent Thevenin's network across resistance R, and obtain current if R is given as 5Ω.		[5]	1	L4	
